
Matthew Loden

ECEN 474


 $Lab\ 08-Operational\ Transconductance\ Amplifier$

Schematic and Pre-lab Simulations:


Schematic:

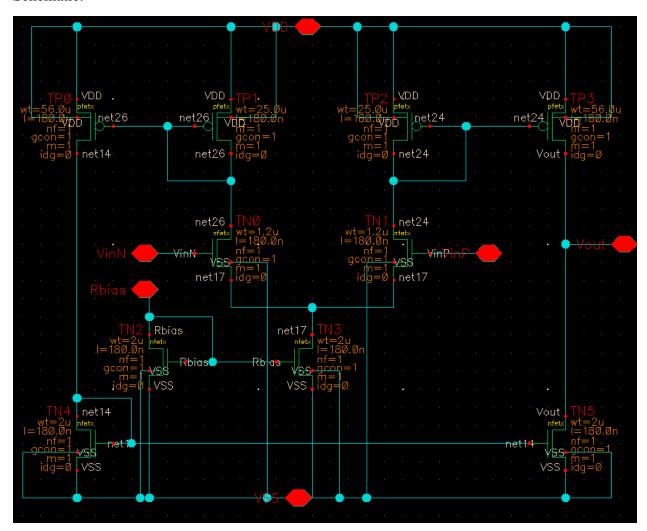


Test Bench:

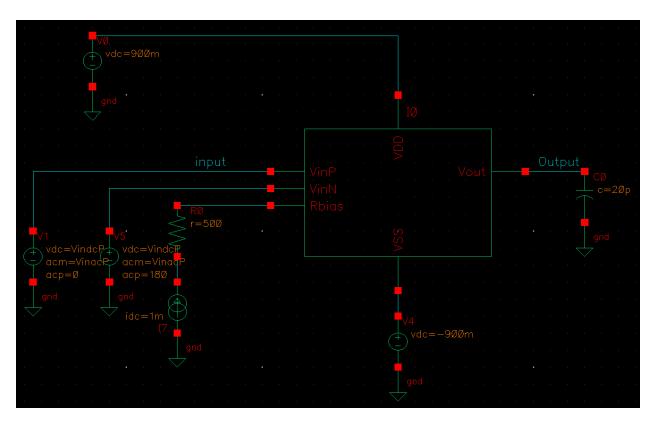

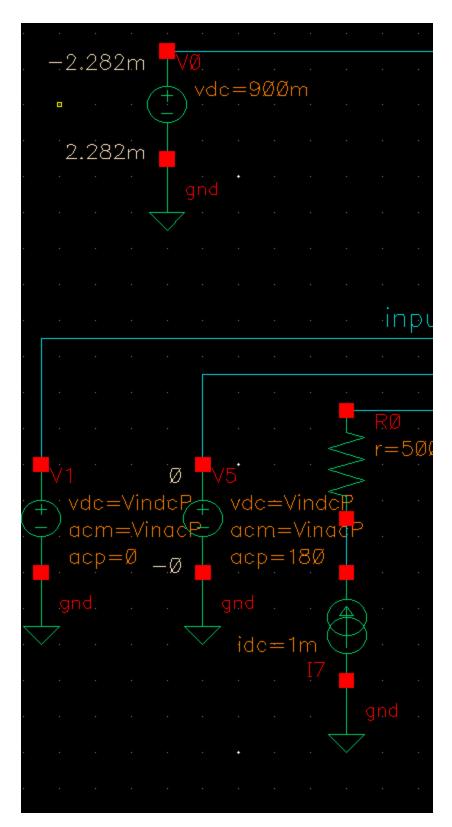Power Draw from Voltage Sources Not Including Current Source:




Power = (2.282-1)mA * 1.8v = 2.307mW

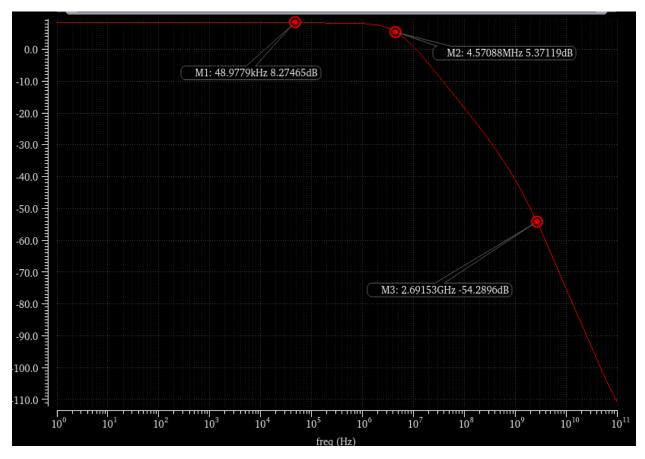


Adm=8.27dB , Dominant Pole = 4.57MHz , Phase margin ensured >60 due to second pole occurring at 2.69GHz which is much larger than three times the pole one frequency.

GBW = Adm * P1 = 11.84MHz

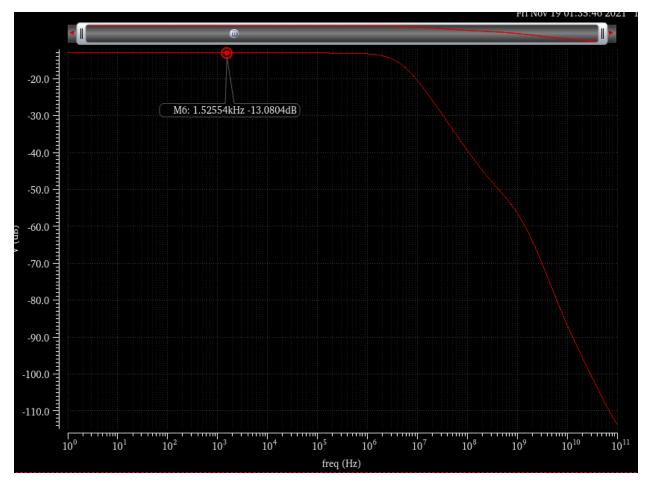


Acm

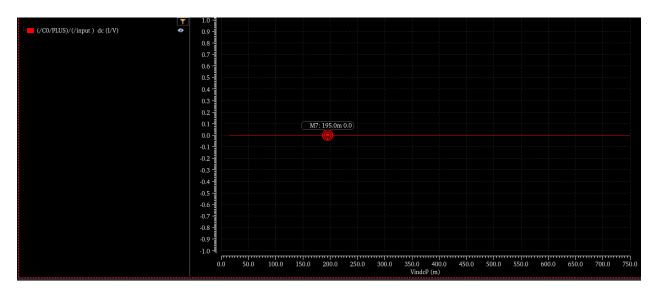


Transconductance

Layout Schematic:

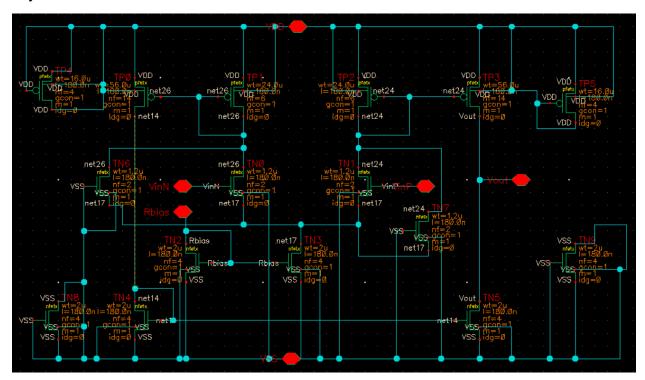


Layout:

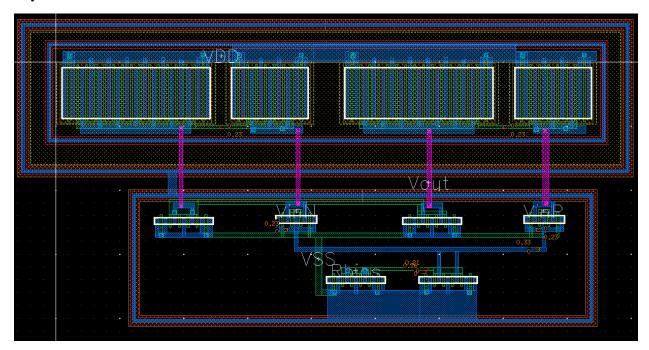


LVS:

REPORT FILE NAME: OTA.lvs.report LAYOUT NAME: /home/ugrads/m/matthewloden/CAL/OTA.sp ('OTA') SOURCE NAME: /home/ugrads/m/matthewloden/LVS/OTA.netlist.lvs ('OTA' RULE FILE: /home/ugrads/m/matthewloden/CAL/_cmhv7sf.lvs.cal_ CREATION TIME: Fri Nov 19 02:56:09 2021 CURRENT DIRECTORY: /home/ugrads/m/matthewloden/CAL USER NAME: matthewloden CALIBRE VERSION: v2020.1_17.9 Fri Jan 3 14:53:07 PST 2020 OVERALL COMPARISON RESULTS CORRECT ################### Warning: Unbalanced smashed mosfets were matched.

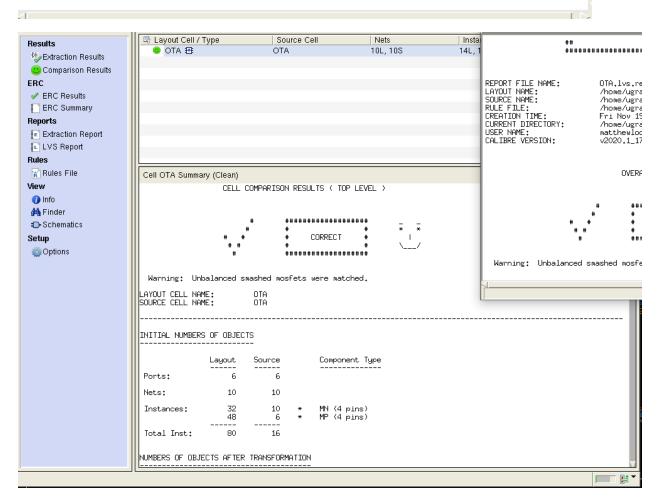

DRC:

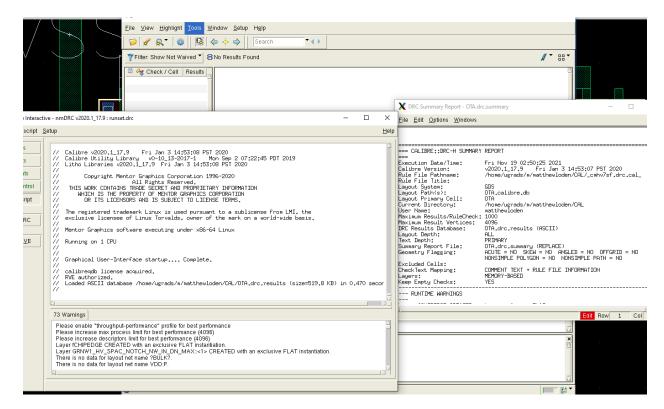

PEX Extraction:




Calibre View generation completed with 1 WARNINGs and 0 ERRORs. Please consult the CIW transcript for messages.


Close

Post Lab Data Calculations and Simulations:


Power Provided by the Voltage Source

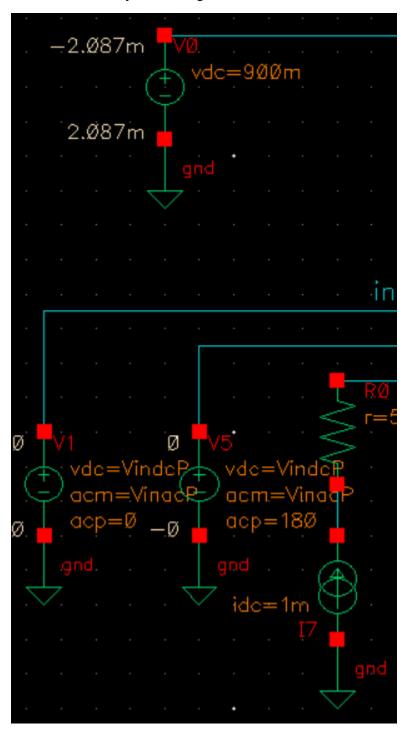

Power = 1.8*(2.087-1) = 1.9566mW

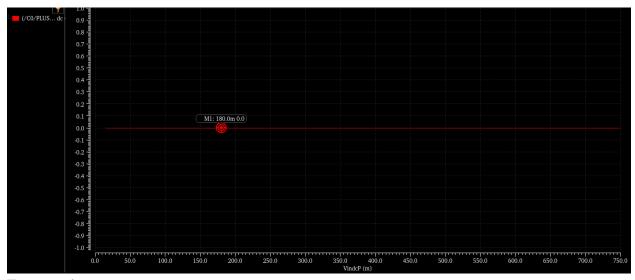


Transconductance

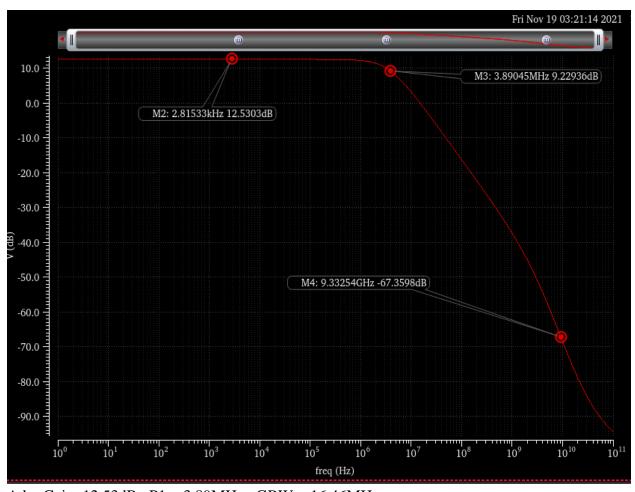

Adm Gain: 12.53dB, P1 = 3.89MHz, GBW = 16.46MHz

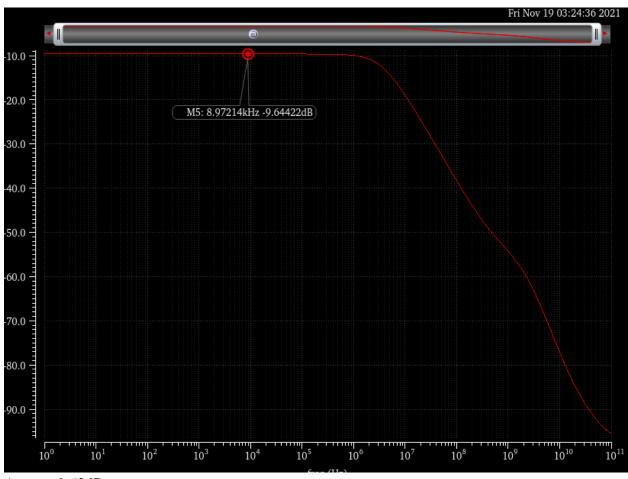P2 = 9.33 GHz, the stability of the system is ensured due to sufficiently large difference from the first pole to the second >> 3factor.



Acm = -9.63dB